

**PAT 451/551**

**INTERACTIVE**

**MEDIA**

**DESIGN I**

**SENSORS**

# SENSING CONTINUOUS CHANGES

- Until now, we've been able to detect *discrete* changes in the environment—buttons that are on or off
  - Digital inputs
  - 0V or 5V signals




- Now, we want to also detect *continuous* variations
  - Analog inputs
  - Signals varying anywhere between 0V and 5V



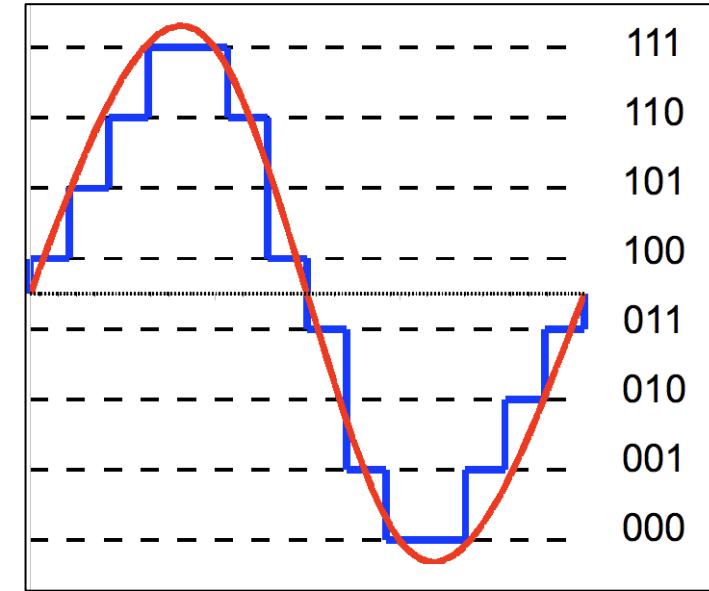
# ANALOG-TO-DIGITAL CONVERSION (ADC)

- **Quantization**
  - Since we have a digital computer, we can only represent a continuously varying voltage as discrete steps.
  - The more steps we have, the closer the approximation to the original signal.




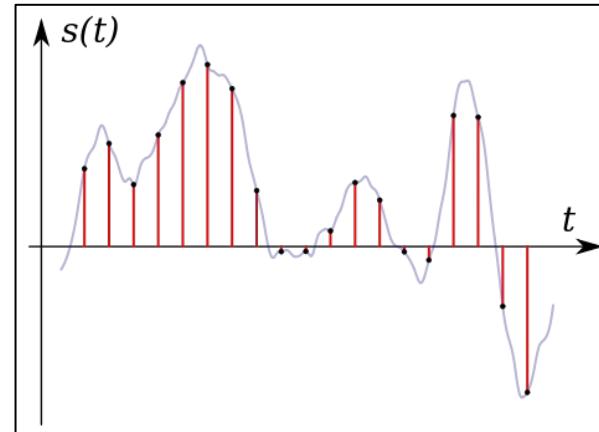- **Sampling**
  - We can only measure at discrete time points
  - Unlike with audio systems, we don't have a fixed sample rate.


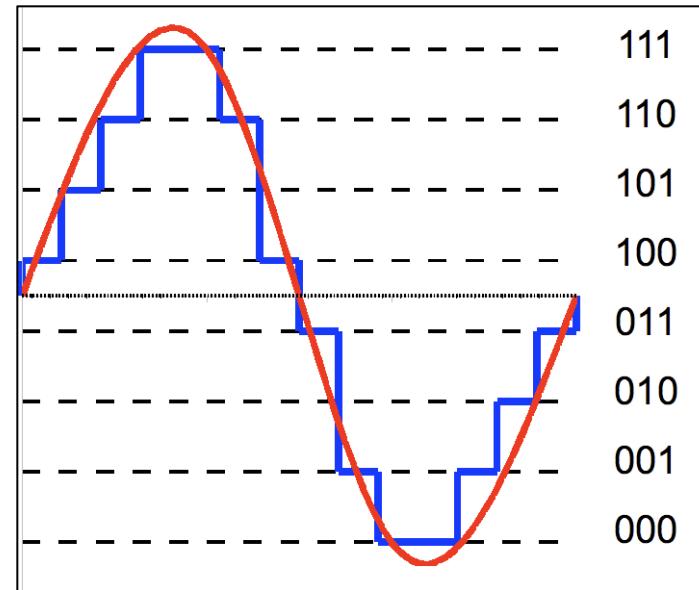
# QUANTIZATION

- Quantization to an **n-bit** number gives  $2^n$  discrete levels
  - Available values are **0 to  $(2^n - 1)$**  if we're only using positive numbers
  - Audio standard: 16-bit (65536 levels)
  - Online image standard: 8 bits (256 levels) per color
  - MIDI data (pitch, velocity, etc): 7 bits (128 levels)
- The **Arduino** has a **14-bit** analog-to-digital converter, so we can represent **16384 levels**, with numbers from 0–16383



**3-bit quantization:**  
8 discrete values,  
0 to 7 (decimal)  
000 to 111 (binary)

# ANALOGREAD FUNCTION

```
int analogRead(pin);
```

By default, `analogRead` uses 10-bit resolution, so it returns a number from 0 to 1023, corresponding to the analog voltage on *pin*.

*pin* is a number from 0 to 5 on the Arduino Uno, corresponding to the numbered analog inputs.

Example usage:

```
int reading = analogRead(0);
```

See **a2dtoSerial.ino** example program.

# VOLTAGE DIVIDER




$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

V is proportional to R, so the voltage drop across R<sub>2</sub> decreases as R<sub>2</sub> gets smaller.

By varying R<sub>1</sub> and/or R<sub>2</sub>, we can vary V<sub>out</sub> while V<sub>in</sub> remains constant.
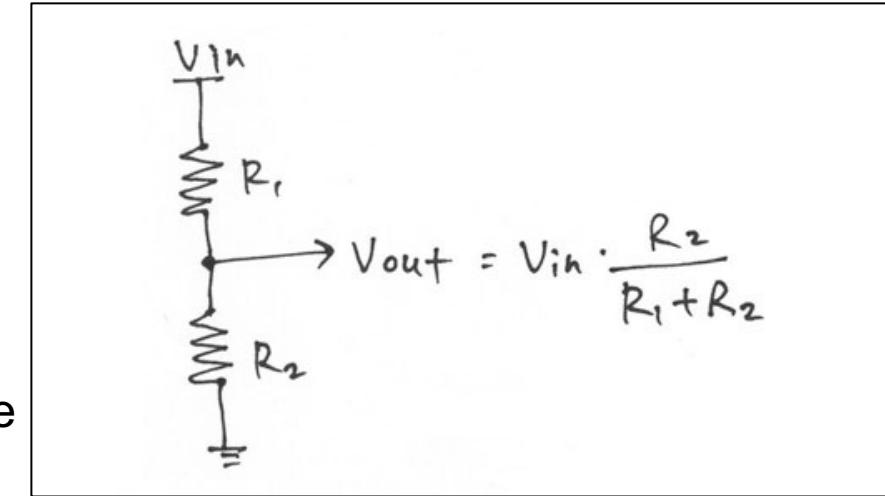
# EXERCISE



- Choose 2 different resistor values and build a voltage divider circuit.
- Measure your resistors.
- Measure your input voltage (should be around 5V).
- Predict what  $V_{out}$  should be based on the measured values.
- Connect  $V_{out}$  to analog input 0 on your Arduino.
- Predict what number should be returned by **analogRead(0)** :  
$$V_{out} / V_{in} * 1024$$
- Run the **a2dtoSerial.ino** example program and compare to your prediction



# ROTATION SENSING

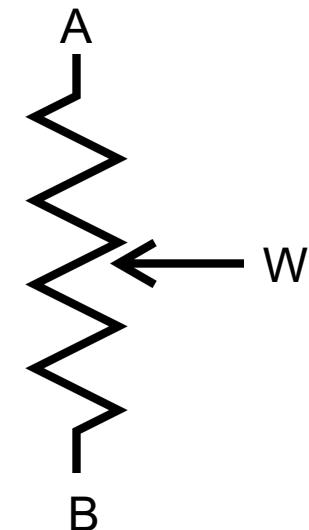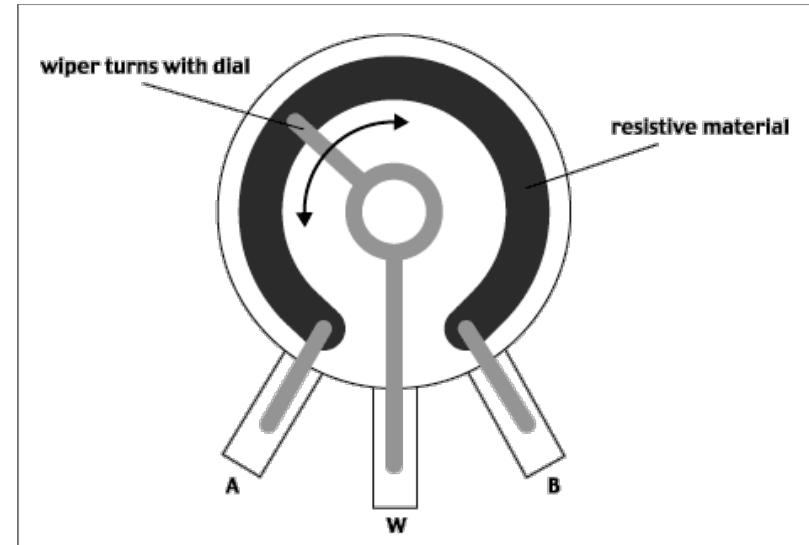
## Potentiometer

- Resistive material
- Wiper moves along material
- Resistance between terminal and wiper varies with distance
- Rotation range is limited by the physical material, usually a bit less than 360°
- Some multi-pots can make more than 1 full rotation, using either a gear mechanism or a spiral resistive element.



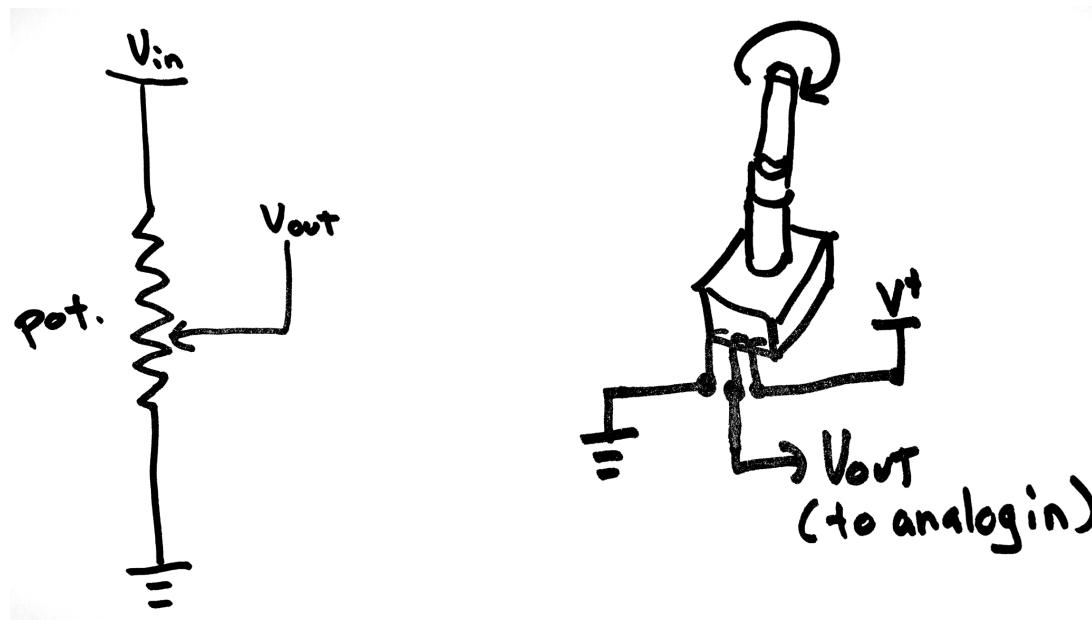
# ROTATION SENSING


- The wiper “divides” the resistance into 2 parts. If we connect the outer legs of the pot to +5V and Gnd, we get a voltage divider.
- $V_{out}$  changes as you rotate the pot.
- Assuming the change in resistance of the material is linear over its length,  $V_{out}$  will vary proportionally to the wiper angle.
- Connect  $V_{out}$  to an **analog input** of the Arduino to measure the voltage





# POTENTIOMETERS

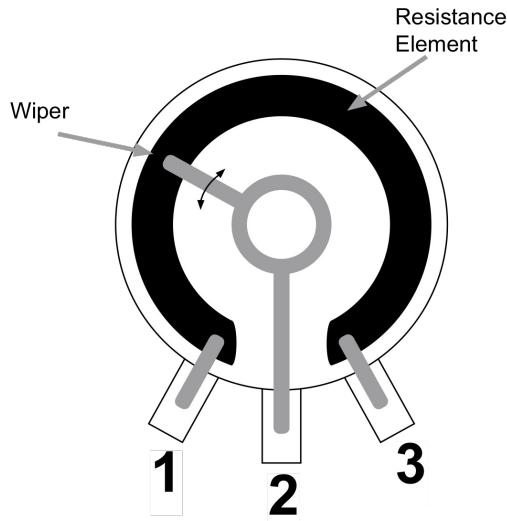

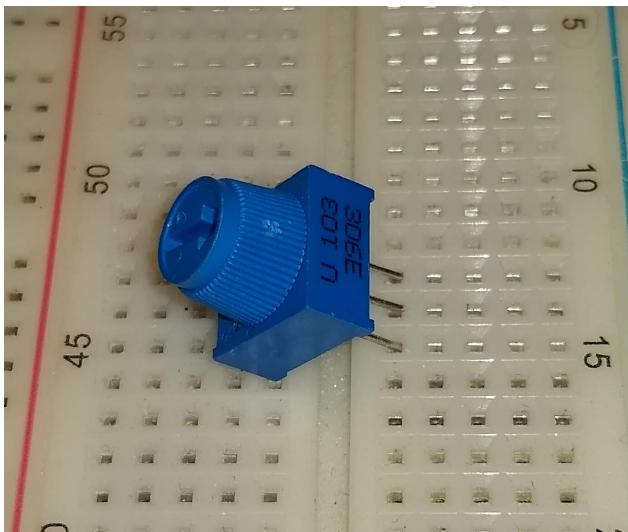
- Pin 2 (middle pin) is always the wiper.
- Pins 1 and 3 are the endpoints.
- The resistance between pins 1 and 3 is constant, and is the rated resistance of the potentiometer.
- Ours are  $10\text{k}\Omega$ .
- These are known as “trimmers” or trimpots.” Handy because they fit into our breadboards.



# POTENTIOMETER CIRCUIT


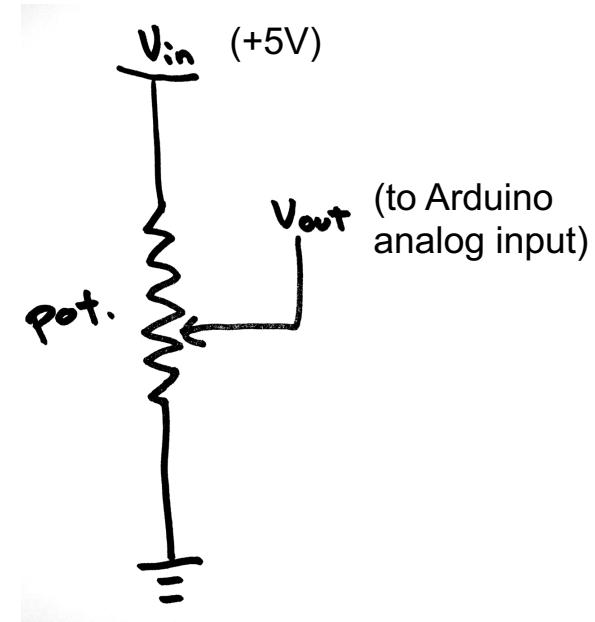
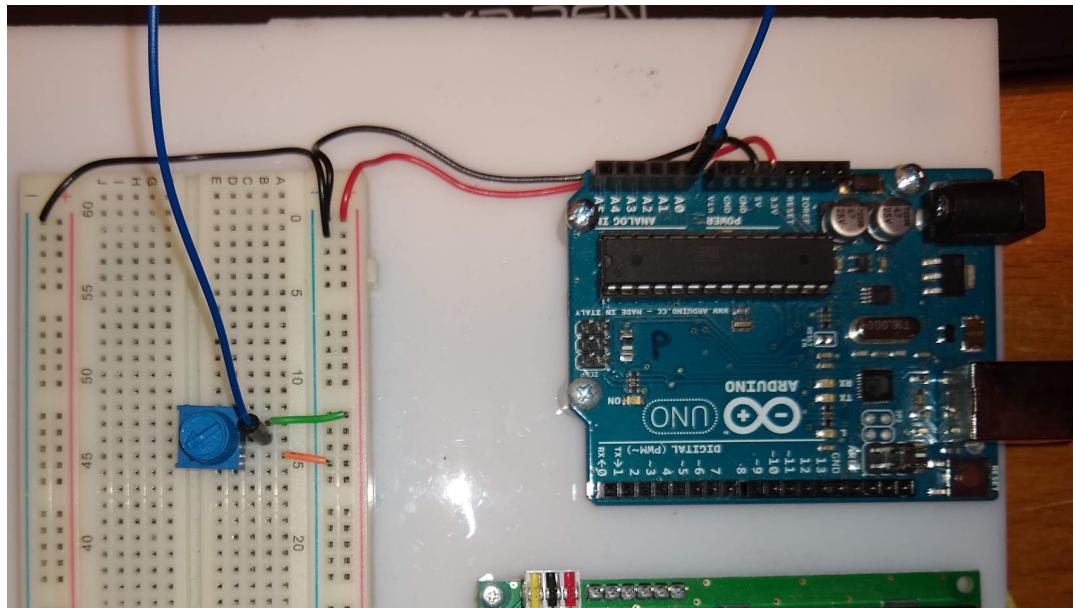


# POTENTIOMETER TAPERS

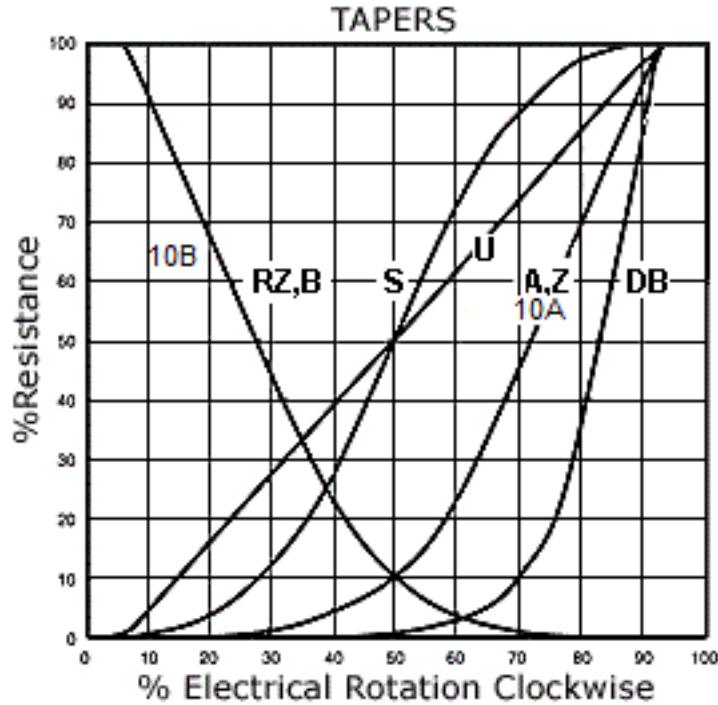


- "Taper" indicates relationship between rotation and resistance in a potentiometer
- Visualized as a curve
- U curve here is linear
- "Audio Taper" or "Log taper" (A,Z) here usually means 10% of the resistance is at 50% rotation. 15% is also common.
  - Designed to represent how we hear changes in loudness for audio circuits.
- When using a pot as a sensor, it's always good to check whether it's linear first.

# OTHER POTENTIOMETER FORMS

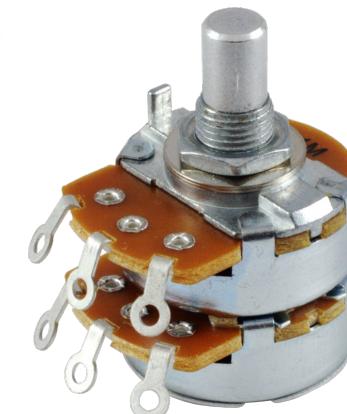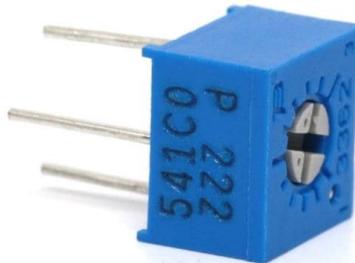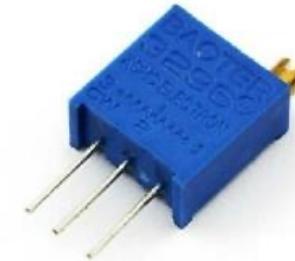

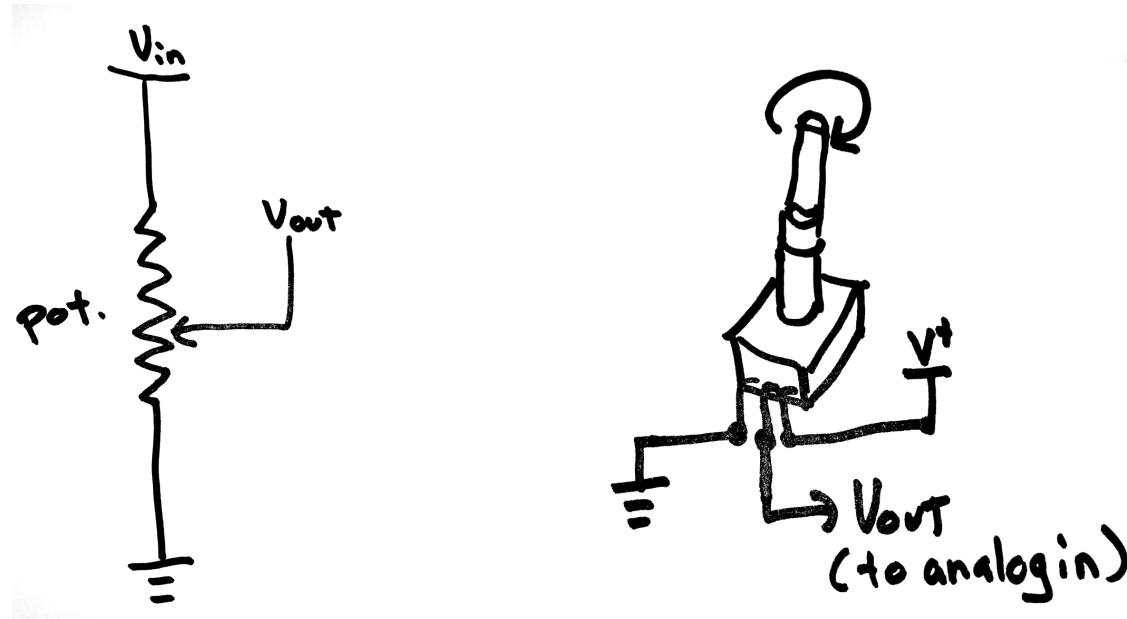
# EXERCISE

- Wire up your blue knob potentiometer as a voltage divider.
- Run the **a2dtoSerial.ino** example program and see the results.
- Does the potentiometer have a linear taper?


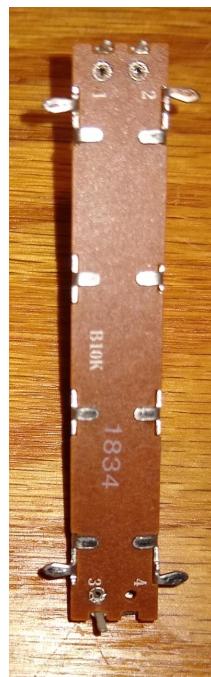
# SLIDE POTENTIOMETER


- Works the same as a rotary pot, except resistive material is arranged in a straight line.
- Can often have audio taper too (think mixing boards)



- Our slide pots have 3 numbered pins on the bottom.
- Pin 2 is the wiper
- Pins 1 and 3 are the fixed endpoints

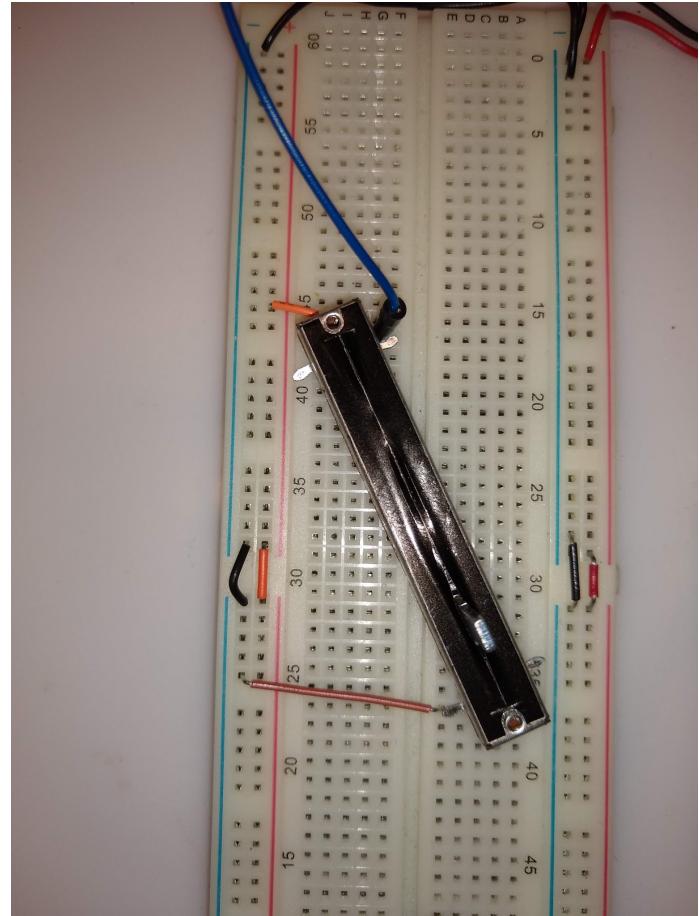
# SLIDE POTENTIOMETER

- Very carefully bend the mounting tabs on the sides of the slide pot upward
- Then you can *very carefully* insert the 3 legs of the pot onto the breadboard, if you mount it at an angle like this.
- Ensure that pins 1 and 2 are in separate rows.
- You might need to *gently* bend one of the pins.




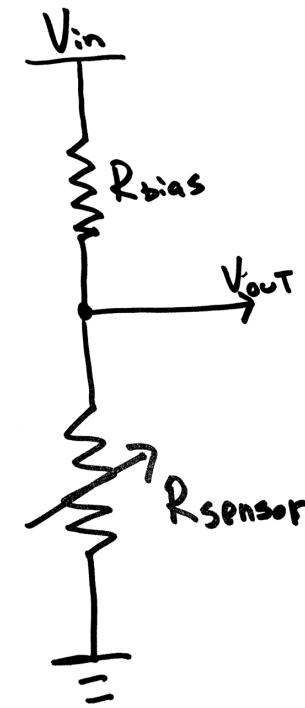
# OTHER RESISTIVE SENSORS

- Some sensors have a **varying resistance** between their 2 leads, depending on some **change in a physical property**
- Need a **fixed resistor** to make a voltage divider: “bias resistor”
- Resistance of the fixed resistor affects **range of output voltage**
- Unless  $R_{\text{sensor}}$  goes from 0 to infinity,  $V_{\text{out}}$  won’t go exactly from 0–5V.




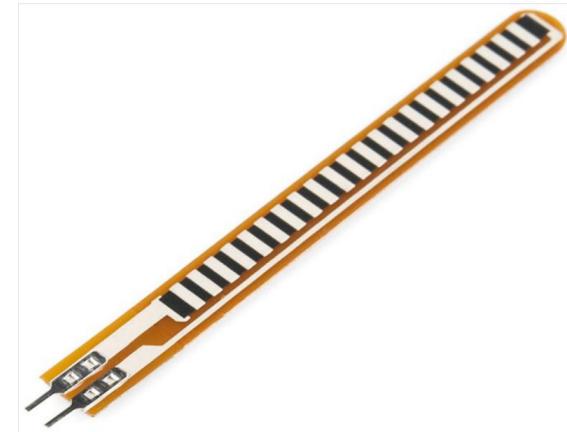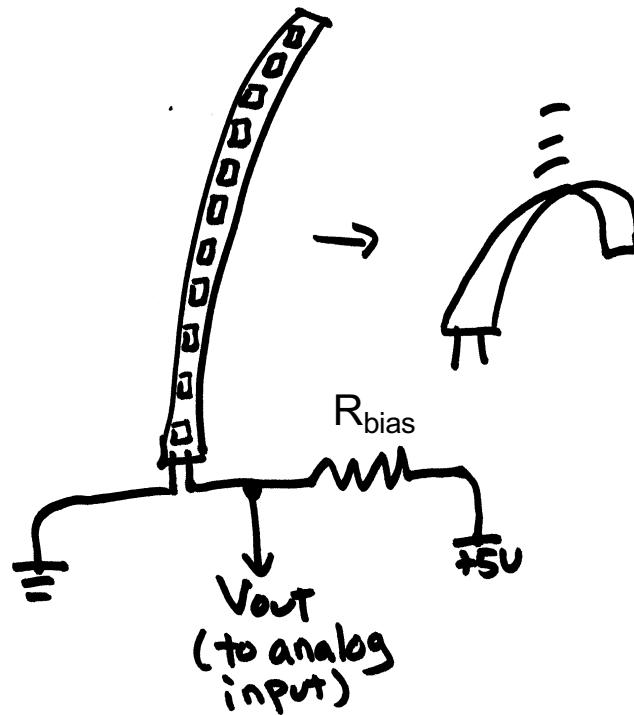
# FLEX SENSOR


- A flex sensor changes resistance as you bend it
- Most sensors only work in 1 direction
- Used in data gloves; sensor is usually finger-length
- Costs about \$10/ea
- Pins are somewhat fragile



# FLEX SENSOR

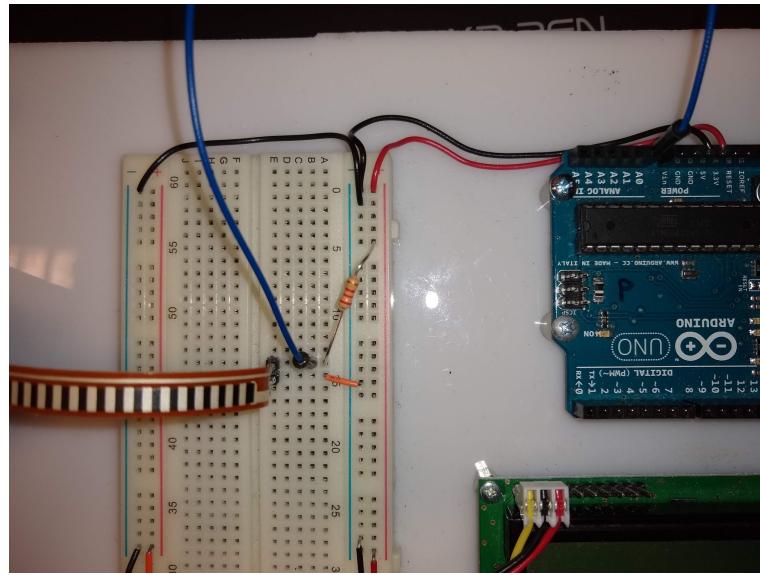
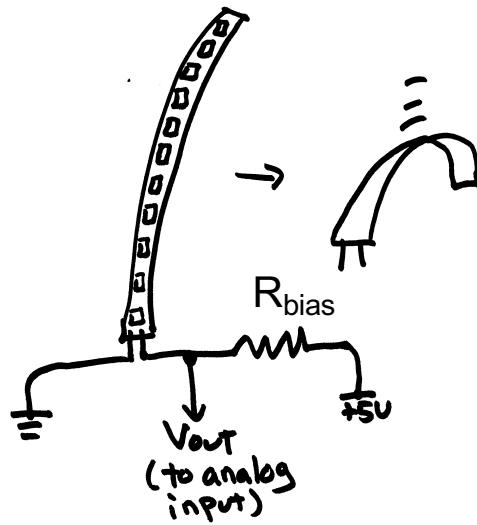


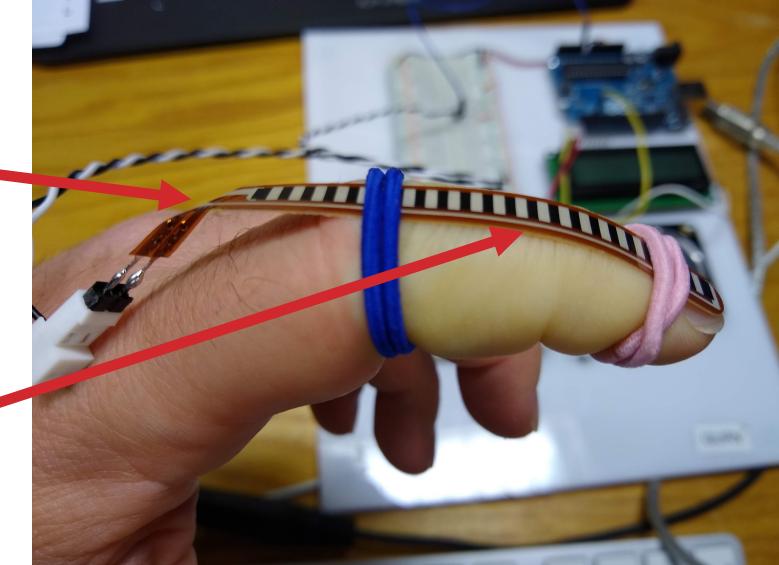Try not to bend this part (pin mounting is fragile)



Bend this part (in the direction shown)

# FORCE SENSING RESISTOR (FSR)

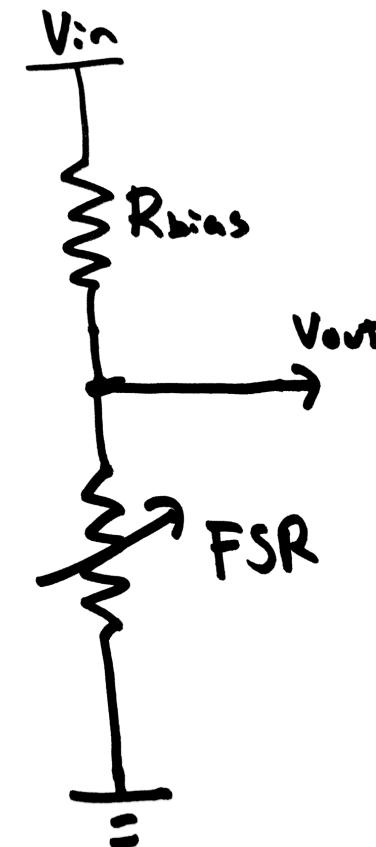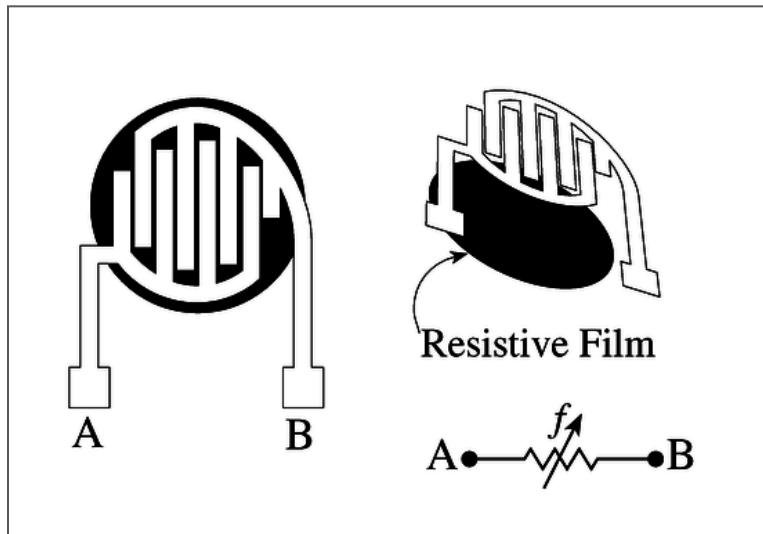



- Resistive polymer film
- Interdigitating contacts
- Resistance inversely proportional to force (resistance goes down as you press harder)

# PHOTOCELL



- AKA: photodetector, photosensor, photo resistor, Light Dependent Resistor (LDR)
- Sometimes known by the semiconductive chemical used: Cadmium Sulfide (CdS)
- Resistance decreases with increasing light intensity
  - Brighter light->less resistance
- Commonly used as a sensor for street lights, garden lights, camera light meters, laser beam-break detector

# PHOTOCELL CIRCUIT

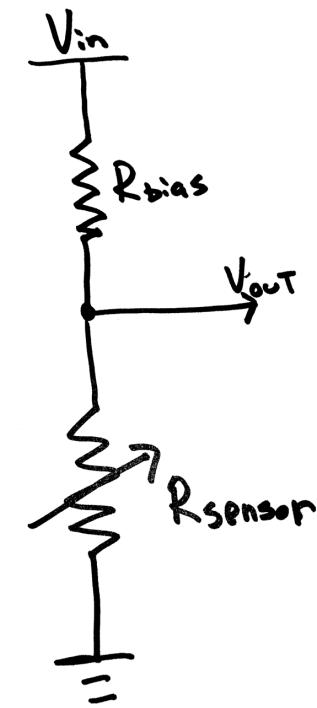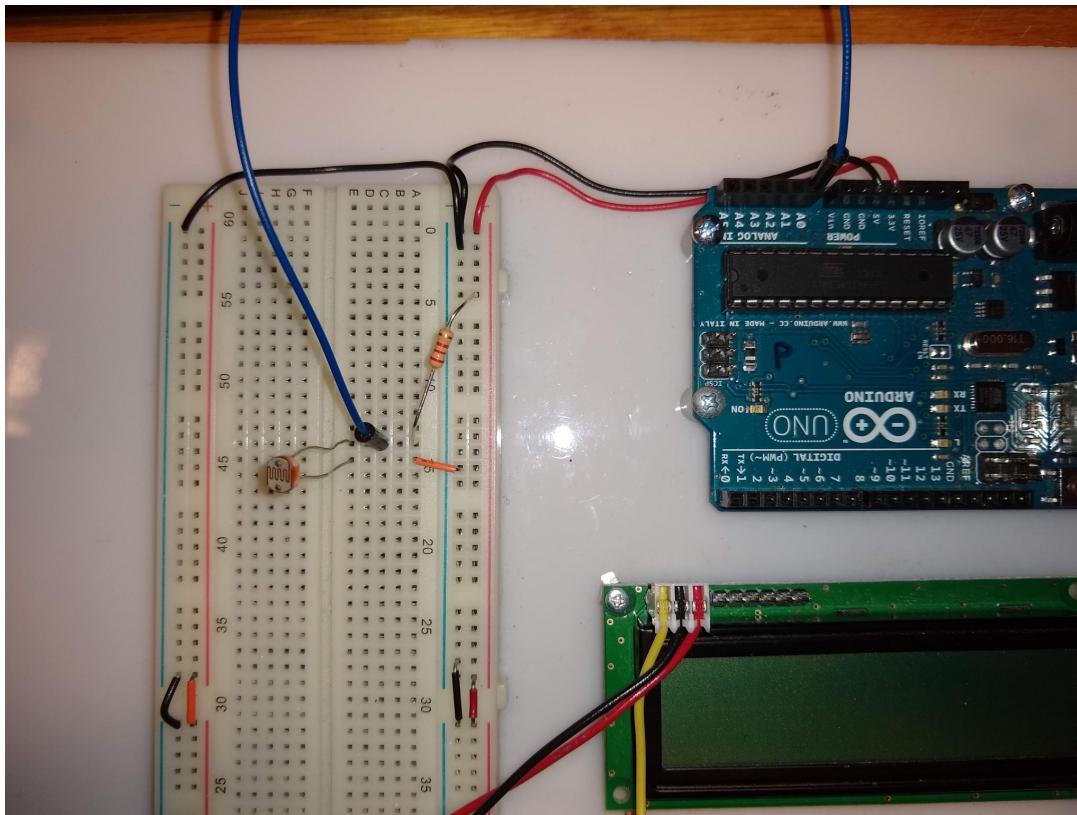

# FINDING THE OPTIMUM BIAS RESISTOR

- Measure the minimum and maximum resistances from your sensor.
- Calculate the geometric mean:

$$R_{bias} = \sqrt{R_{min} \cdot R_{max}}$$

- Find the closest resistor you can.
- If you need something precise, you can always use 2 or more resistors in series.
- Calculate the minimum and maximum voltages you expect:

$$V_{min} = 5 \frac{R_{min}}{R_{min} + R_{bias}}$$

$$V_{max} = 5 \frac{R_{max}}{R_{max} + R_{bias}}$$

# EXAMPLE

- Measure the minimum and maximum resistances from your sensor.
- Calculate the geometric mean:

$$R_{bias} = \sqrt{1502 \cdot 18270}$$

$$R_{bias} = 5238\Omega$$

- Find the closest resistor you can:




Green-blue-red-gold: 5.6 kΩ


- Calculate the minimum and maximum voltages you expect:

$$V_{min} = 5 \frac{R_{min}}{R_{min} + R_{bias}} = 5 \frac{1502}{1502 + 5600} = 1.06V$$
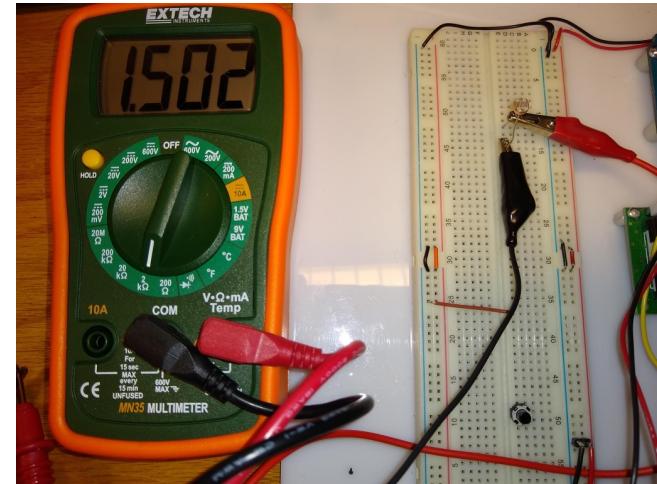
$$V_{max} = 5 \frac{R_{max}}{R_{max} + R_{bias}} = 5 \frac{18270}{18270 + 5600} = 3.83V$$



$$R_{min} = 1.502k\Omega$$

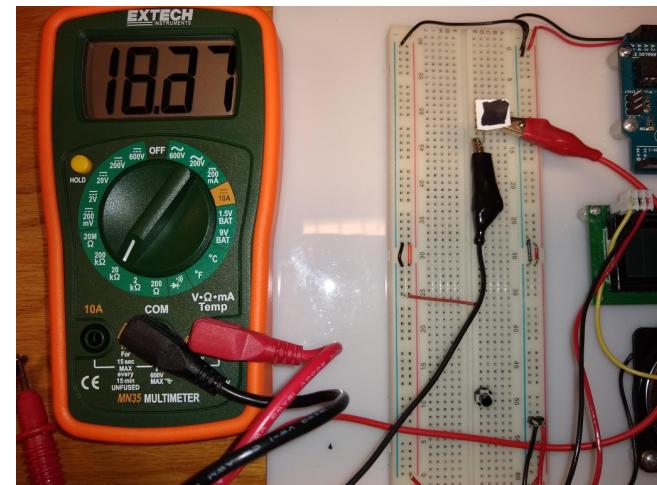

$$R_{max} = 18.27k\Omega$$

# EXAMPLE

- Now calculate predicted values returned by `analogRead()` :

$$1024 * \frac{1.06V}{5V} = 217$$

$$1024 * \frac{3.83V}{5V} = 784$$


- So we should expect to see values in the range of 217–784 in the Serial monitor.
- Take note: in the future, when we want to control things (i.e. music parameters) with these data, it's useful to know what range of values we should get, and not just guess.

# ANALOG-TO-DIGITAL CONVERSION: SUCCESSIVE APPROXIMATION

- Define  $n$  bits  $B_0$  to  $B_{n-1}$ 
  - Each bit can have the value 1 or 0
  - $B_{n-1}$  is the MSB;  $B_0$  is the LSB
- Initialize all bits to 0
- **For each value of  $k$  from 1 to  $n$ :**
  - Temporarily set  $B_{n-k}$  to 1
  - Calculate  $V_{COM}$ :  
$$V_{COM} = V_{REF} \left[ \frac{B_{n-1}}{2^1} + \frac{B_{n-2}}{2^2} + \frac{B_{n-3}}{2^3} + \dots \right]$$

(Initially, this is just  $V_{ref} / 2$ )
  - If  $V_{in} > V_{COM}$ : keep  $B_{n-k}$  at 1
  - If  $V_{in} < V_{COM}$ : set  $B_{n-k}$  to 0
  - Repeat

# ANALOG-TO-DIGITAL CONVERSION

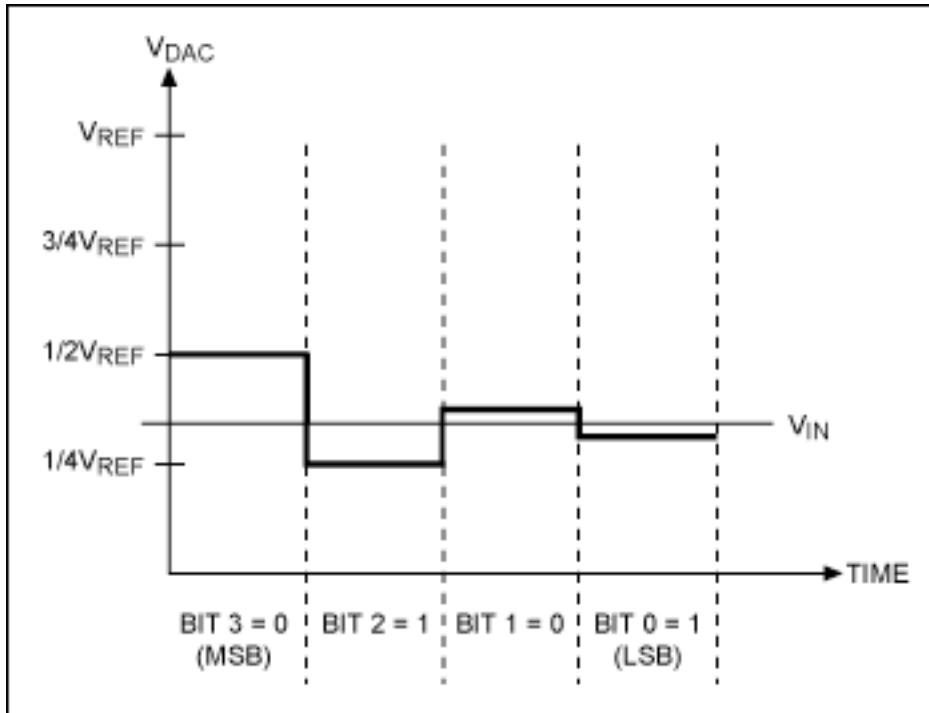

- Successive Approximation 4-bit ADC example

$k = 1$ :

- $V_{COM} = V_{REF} / 2$
- $V_{in} < V_{COM}$
- $B_3$  is 0

$k = 2$ :

- $V_{COM} = V_{REF} / 4$
- $V_{in} > V_{COM}$
- $B_2$  is 1


$k = 3$ :

- $V_{COM} = V_{REF} / 4 + V_{REF} / 8$
- $V_{in} < V_{COM}$
- $B_1$  is 0

$k = 4$ :

- $V_{COM} = V_{REF} / 4 + V_{REF} / 16$
- $V_{in} > V_{COM}$
- $B_0$  is 1

# ANALOG-TO-DIGITAL CONVERSION

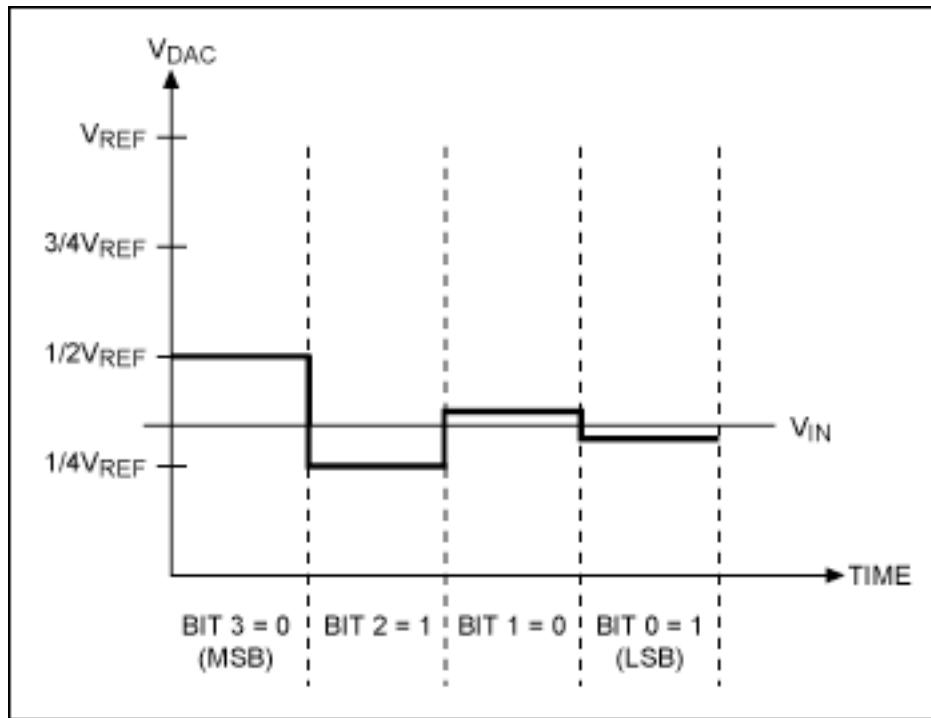

The Resulting Binary Number Is:

0 1 0 1

$$= 0*2^3 + 1*2^2 + 0*2^1 + 1*2^0$$

$$= 0 + 4 + 0 + 1$$

$$= 5$$

Maximum value is  $2^4 - 1 = 15$

- Successive Approximation 4-bit ADC example

# ANALOGREAD RESOLUTION

```
int analogReadResolution(int);
```

By default, `analogRead` uses 10-bit resolution. This can be increased to 12-bit or 14-bit on several Arduino devices by passing the argument 12 or 14.

`analogRead()` will then return numbers in the range of 0–4095 for 12-bit and 0–16383 for 14-bit resolution

# MAP FUNCTION FOR LINEAR SCALING

```
long map(value, fromLow, fromHi, toLow, toHi);
```

*map* linearly scales the number *val* in the range of *fromLow* – *fromHi* to a number in the range of *toLow* – *toHi*

It does not limit the input or output to be in the ranges specified.

It uses integer math, so values may be truncated or subject to rounding errors.