

PAT 451/551

INTERACTIVE

MEDIA

DESIGN I

**MOSFETS: CONTROLLING HIGH-POWER
DEVICES**

GENERAL PRINCIPLE

POWER

to the device is supplied externally (NOT from the Arduino)

- For DC devices, from a wall-wart or other DC power supply
- For AC devices, from AC mains power outlet


A chip or controller

allows the Arduino to switch on/off the current flow to that device using a low-voltage control signal

Why?

Arduino digital I/O pins can only sink/source 40mA. Most devices like motors, lights, solenoids require much more power than that.

GENERAL PRINCIPLE

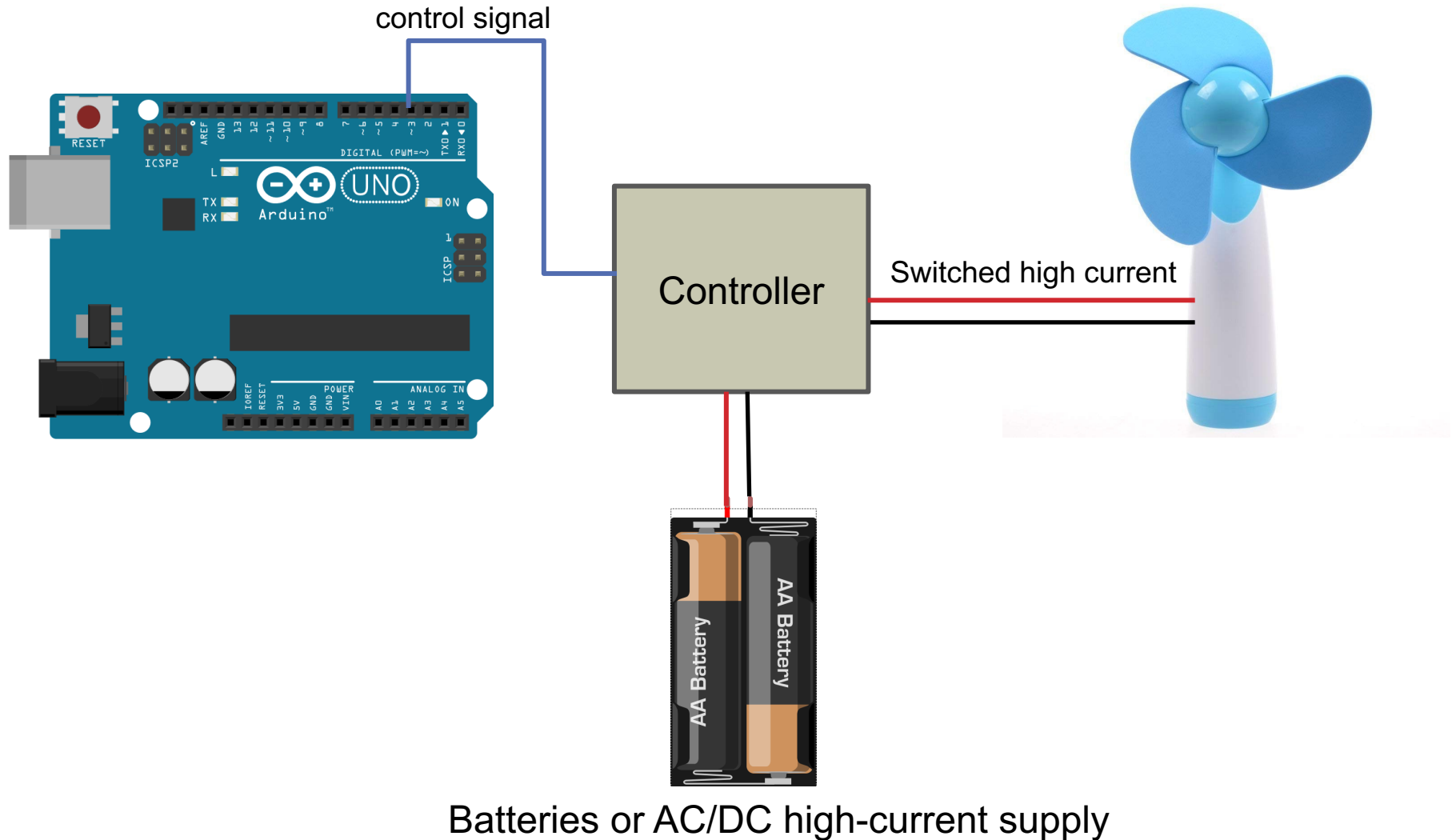

CONTROLLER TYPES

Transistor

- Simplest for digital/binary on/off control
- DC devices only, current/load limited
- Fast switching, can be held on/off indefinitely
- Potentially noisy for continuous control
- No direction control for motors

H-Bridge

- Designed for motor control
- Usually used on a separate controller board
- Most can power 2 motors, direction and speed control
- DC or Stepper motors

Relay



- For intermittent switching; can't be held indefinitely
- Can handle higher loads/current than transistors
- AC or DC versions
- Electromechanical or Transistor-based control

ARDUINO POWER ARCHITECTURE

V_in pin carries whatever voltage is supplied on the **barrel jack connector (red)**

5V Pin carries a 5V, either from the **Buck Converter** or **USB**

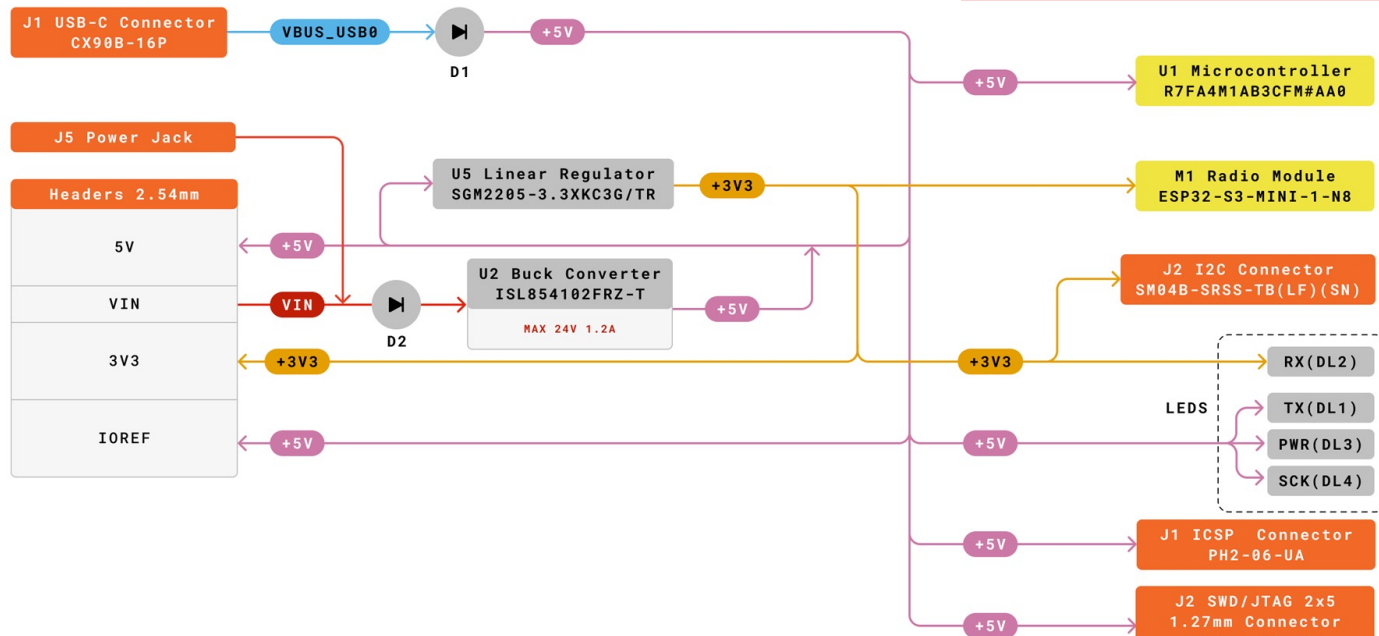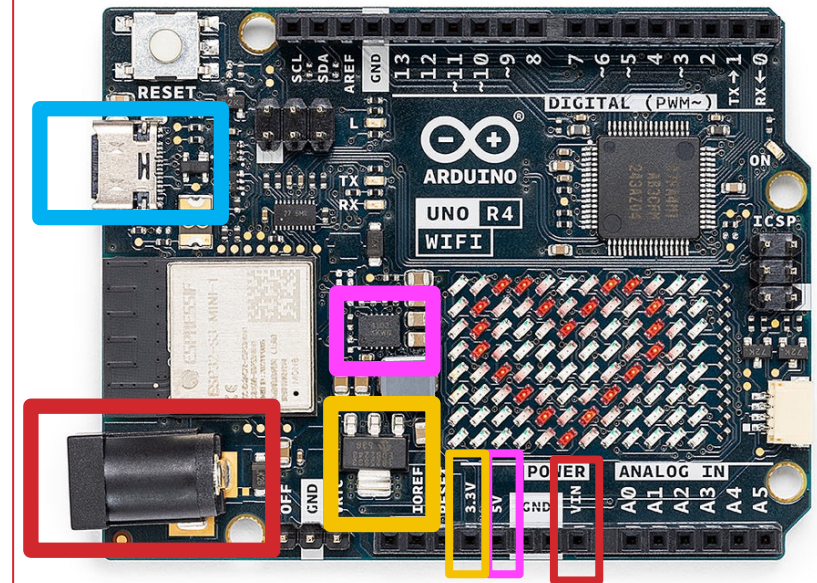3.3V Pin carries 3.3V from a **voltage regulator**



ARDUINO POWER ARCHITECTURE


Barrel jack connector:

Must be 5-24V DC


center positive 

If $V_{in} > 6.6V$, that voltage will be used to power the Arduino

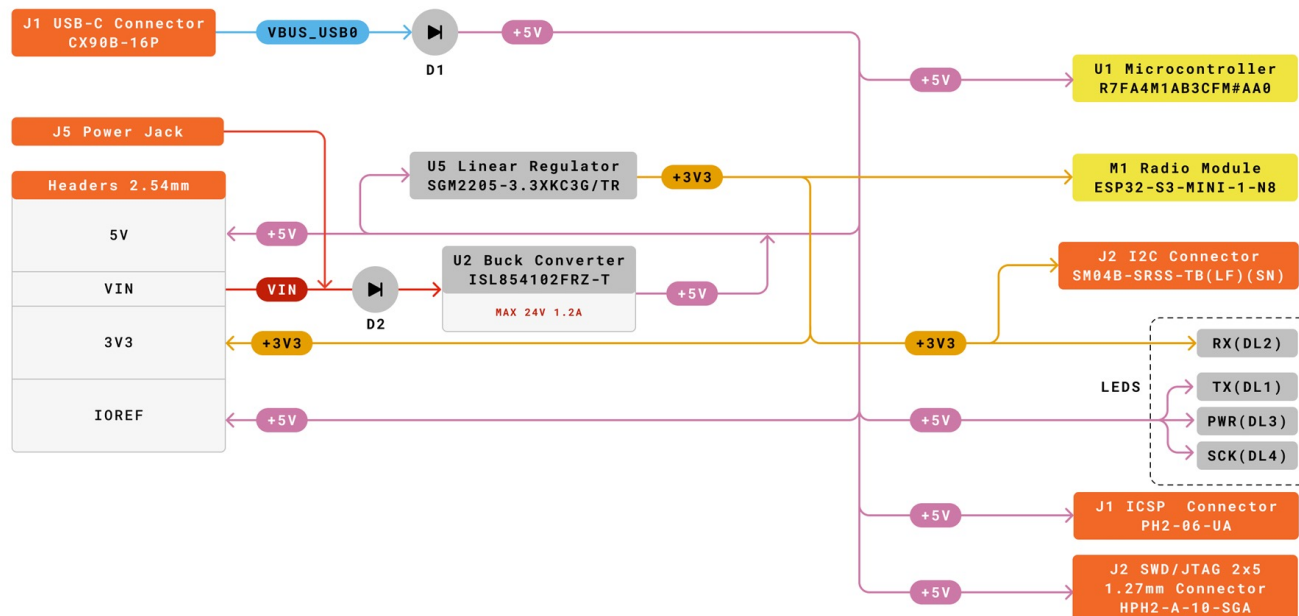If $V_{in} < 6.6V$, the 5V USB power will be used to power the Arduino



USING ARDUINO VIN

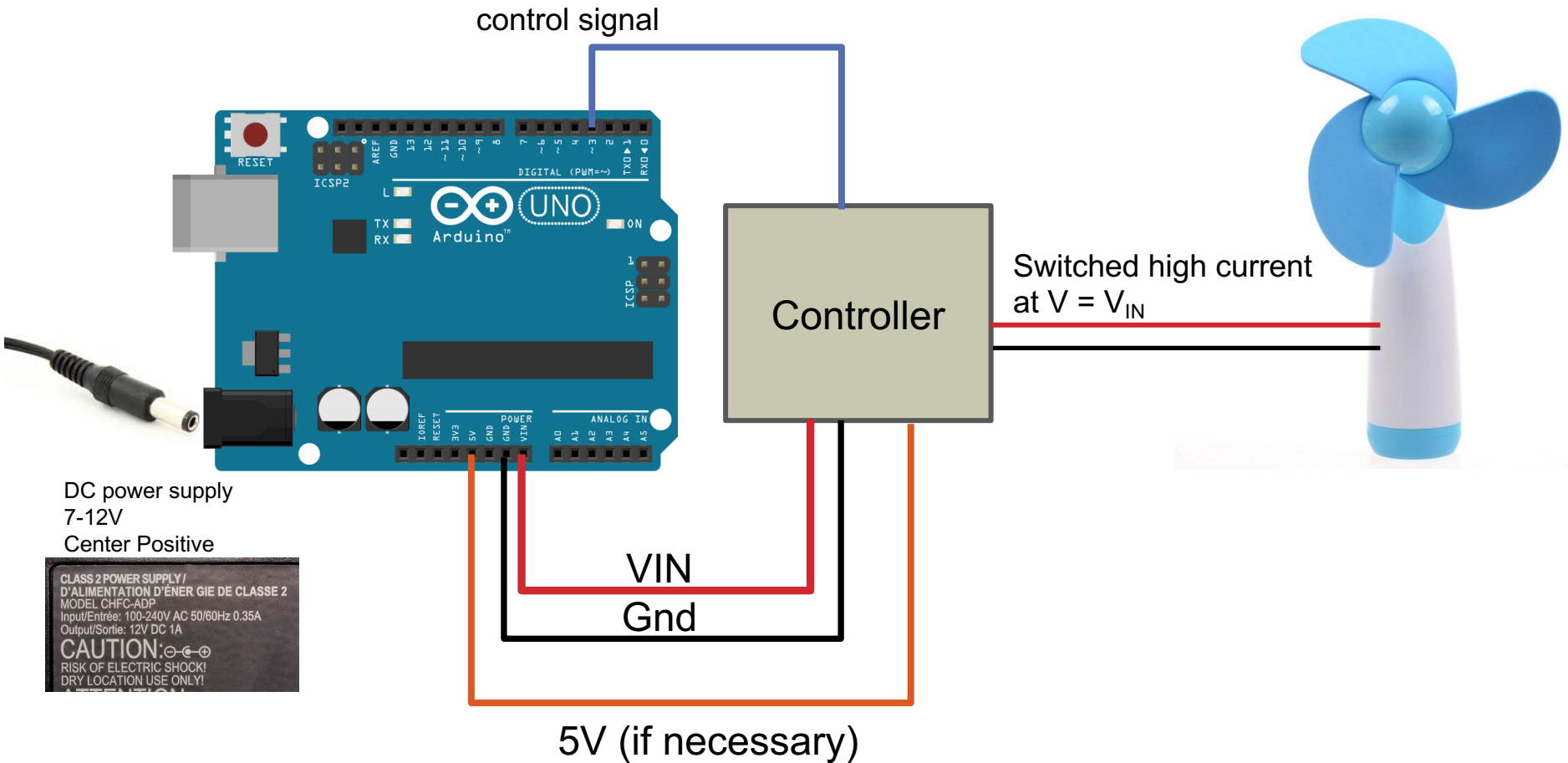

TRANSISTORS



For a full tutorial, see: <https://learn.sparkfun.com/tutorials/transistors/all>

Two basic varieties: NPN and PNP



B = Base

C = Collector

E = Emitter

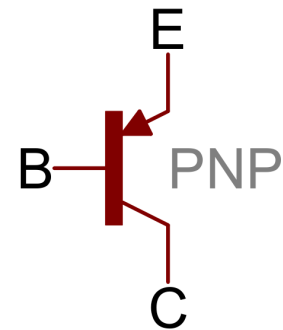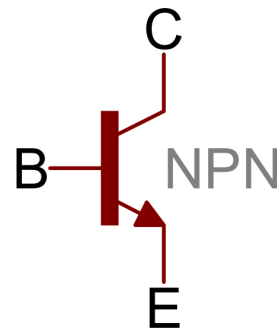


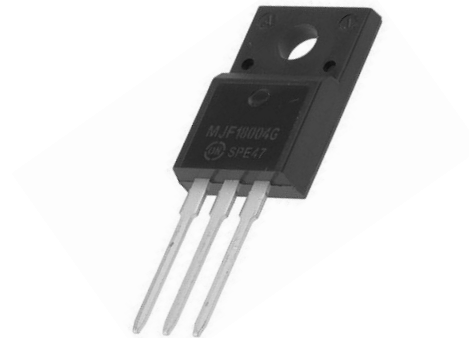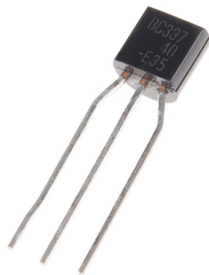Most crudely, the base voltage controls current flow from the collector to the emitter.



TRANSISTORS

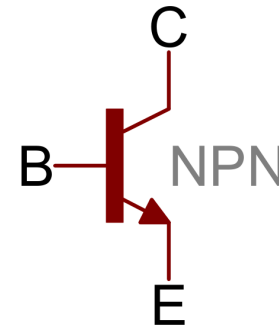We'll most commonly use an NPN transistor



It has 4 modes, based on the relationship of the 3 voltages at C, B, and E

1. Saturation Mode: $V_E < V_B$ and $V_C < V_B$

- Transistor acts like a **short circuit** — current flows freely from C to E

2. Cut-off Mode: $V_E > V_B$ and $V_C > V_B$

- Transistor acts like an **open circuit** — no current flows

3. Active Mode: $V_C > V_B > V_E$

- Transistor acts like an *amplifier* — current from C to E is *proportional to* current flowing into the base


4. Reverse Active Mode: $V_C < V_B < V_E$

- Transistor acts like a *reverse amplifier* — current from E to C is *proportional to* current flowing into the base (rarely used)

TRANSISTOR AS SWITCH

When Control signal is at 5V, transistor is in **Saturation Mode** ($V_E < V_B$ and $V_C < V_B$): transistor acts as a **short circuit**.

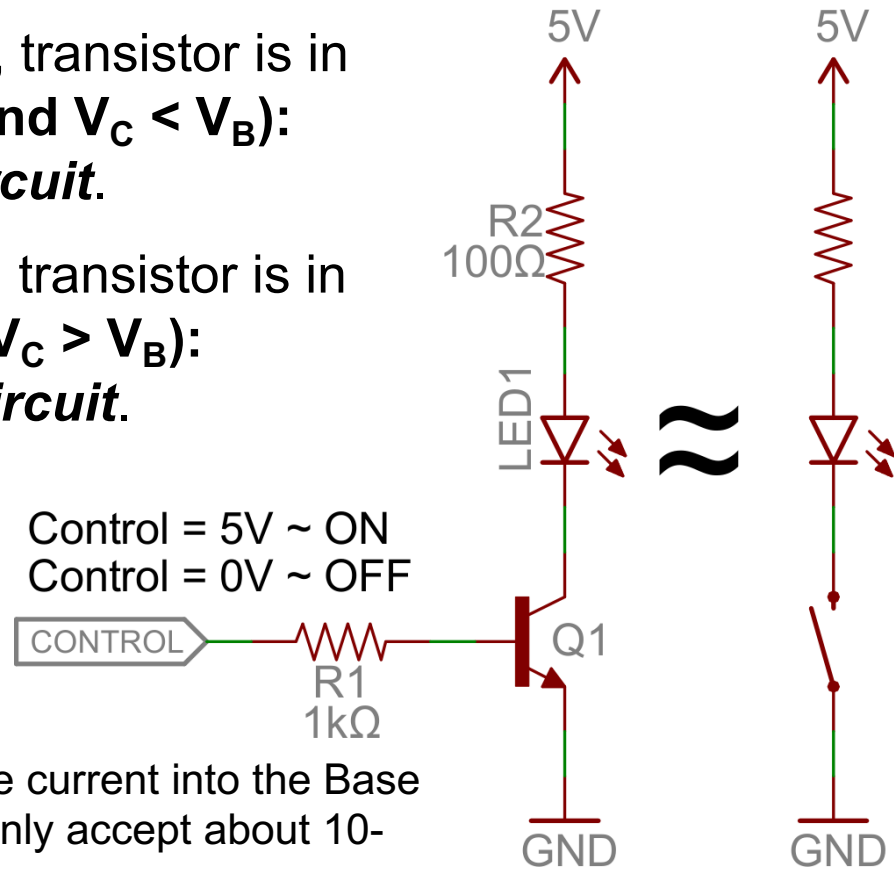When Control signal is at 0V, transistor is in **Cut-off Mode** ($V_E > V_B$ and $V_C > V_B$): transistor acts as an **open circuit**.



R1 is needed here to limit the current into the Base of the Transistor. It can only accept about 10-100mA of current

MOSFETS

Tutorial Here! https://youtu.be/CFt8hkh17_w

The Transistors we've looked at are technically

Bipolar Junction Transistors (BJT)

Most modern power applications use

Metal-Oxide Field-Effect Transistors (MOSFET)

The principles are the same, but we replace

Base (B) with Gate (G)



Collector (C) with Source (S)

Emitter (E) with Drain (D)

NPN BJT ~~ N-Channel MOSFET

PNP BJT ~~ P-Channel MOSFET

MOSFET AS SWITCH

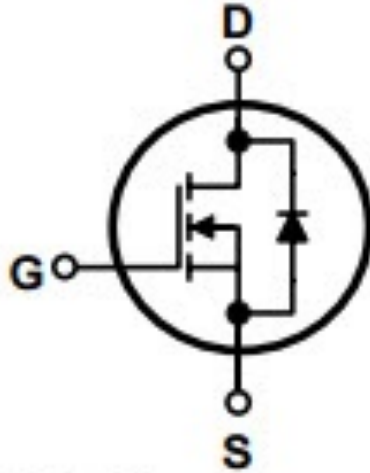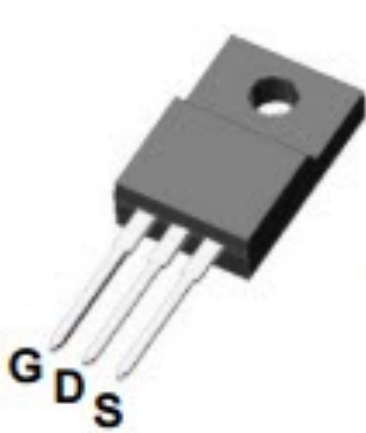


If $V_{\text{gate}} > V_{\text{source}}$ current flows from D to S
(short circuit)


If $V_{\text{gate}} \leq V_{\text{source}}$ no current flows from D to S
(open circuit)

N channel MOSFET Pinout

N-CHANNEL MOSFET AS SWITCH


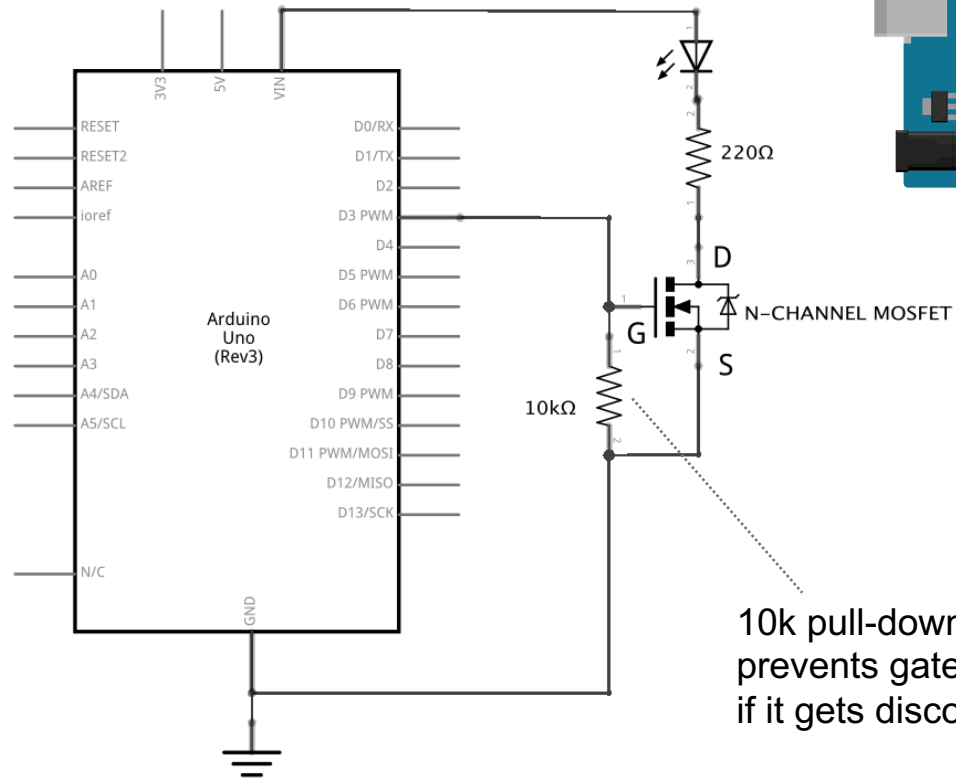


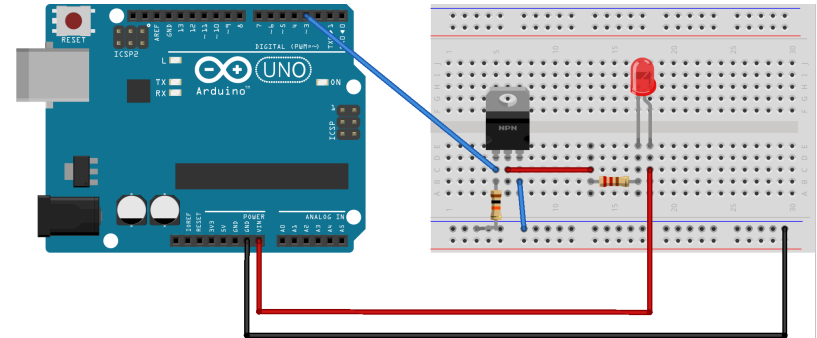10k pull-down resistor prevents gate voltage from floating if it gets disconnected



N-CHANNEL MOSFET AS MOTOR DRIVER

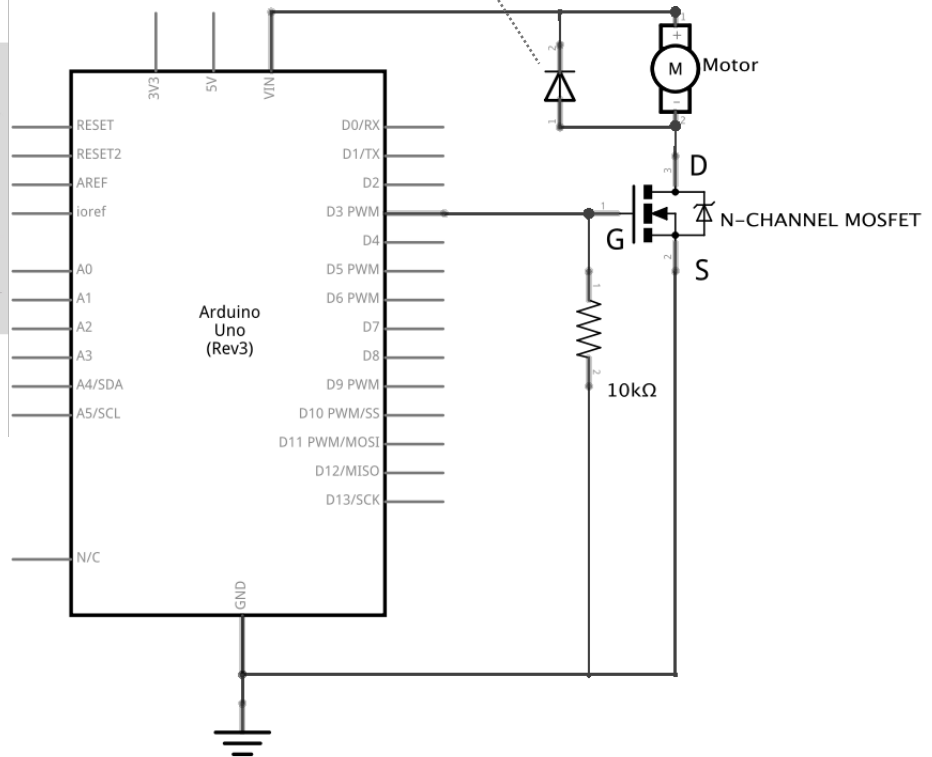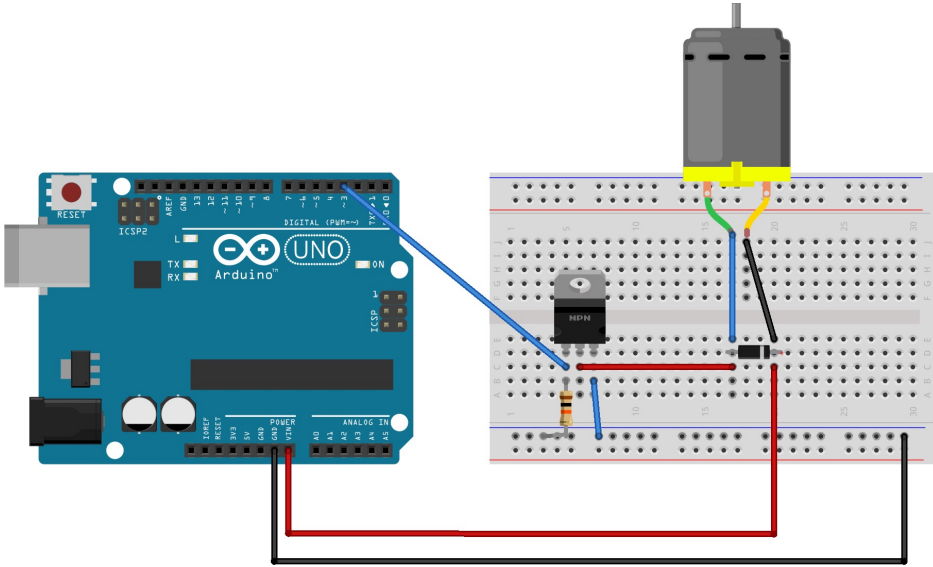“flyback” diode dissipates backward current flow from shutdown spikes (happens with motors and solenoids)



OTHER RESOURCES

Sparkfun Transistor Tutorial:

<https://learn.sparkfun.com/tutorials/transistors/all>

Make: Electronics, Chap. 2:

<https://search.lib.umich.edu/catalog/record/99187290028506381>

Relays:

<https://learn.adafruit.com/adafruit-power-relay-featherwing>

<https://howtomechatronics.com/tutorials/arduino/control-high-voltage-devices-arduino-relay-tutorial/>